Capacitors we used are electrolytic rated at 400 volts x 47 uF put in series to equal 6,000 volts, the diodes we used were silicon 1000 volt 2 amp placed in series to equal 6,000 volts........ Ground was connected to laboratory wall out let ground.

If you decide to try Tesla's experiment by pumping DC into the ground be careful, I tried this and it does work but is very dangerous to you or your neighbors. If someone is taking a shower or using water they can get killed or shocked. do this experiment far away from humans and animals, you can get far more energy out than you put in. I will not tell you much more because it is such a dangerous experiment. Capacitor Bank Meter or Load